

III B. Tech I Semester Regular/Supplementary Examinations, October/November - 2019
DIGITAL IC APPLICATIONS

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**

PART -A

(14 Marks)

1. a) What is fan-in and fan-out? [2M]
- b) Write down the syntax of a VHDL entity declaration. [2M]
- c) What do you mean by concurrent statement? [2M]
- d) Briefly discuss about priority encoder. [3M]
- e) What is race around condition? How it is avoided? [3M]
- f) What is timing diagram? [2M]

PART -B

(56 Marks)

2. a) Which bipolar family is best suited for LSI? Show the circuit of a 4-input NAND gate using CMOS transistors. [7M]
- b) List out the family members of TTL family. Write down the typical values of characteristics of all the TTL series. [7M]
3. a) With suitable block diagram explain about the design flow of VHDL. [7M]
- b) Explain the various scalar data types supported by VHDL with suitable examples. [7M]
4. a) With suitable example, explain PROCESS statement in VHDL. [7M]
- b) List out the differences between inertial delay model and transport delay model with example. [7M]
5. a) Write a VHDL program for 16-bit barrel shifter for left circular shift only? [7M]
- b) Write a VHDL code for four bit parallel adder/subtractor. [7M]
6. a) Discuss the logic circuit of 74 x 377 register. Write a VHDL program for the same in structural style. [7M]
- b) Design a 4-bit binary synchronous counter using 74x74. [7M]
7. a) What are the Moore and Mealy machines? Compare them. [7M]
- b) For the machine given in table, find the equivalence partition and a corresponding reduced machine in standard form and also explain the procedure. [7M]

PS	NS,Z	
	X=0	X=1
A	B, 0	E, 0
B	E, 0	D, 0
C	D, 1	A, 0
D	C, 1	E, 0
E	B, 0	D, 0

III B. Tech I Semester Regular/Supplementary Examinations, October/November - 2019
DIGITAL IC APPLICATIONS

(Common to Electronics and Communication Engineering, Electronics and Instrumentation Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**

PART –A

(14 Marks)

1. a) State the noise margin for CMOS family. [2M]
- b) List out the different operators in VHDL. [3M]
- c) What do you mean by sensitivity list? [2M]
- d) What do you mean by comparator? [2M]
- e) List out the differences between asynchronous counter and synchronous counter. [3M]
- f) What is state assignment? [2M]

PART –B

(56 Marks)

2. a) Explain what is mean by logic family? Construct an Ex-NOR circuit using CMOS transistors and explain its operation. [7M]
- b) Explain the difference between current sinking and current sourcing logic circuits. How are they estimated for CMOS families? [7M]
3. a) What is package body? Explain with example. [7M]
- b) With the help of block diagram explain the program structure of VHDL. [7M]
4. a) Explain CASE statement in VHDL with example. [7M]
- b) List out the differences between variable assignment statement and signal assignment statement with example. [7M]
5. a) Design a function $F = ABC + (A+B+C)'$ by using 74X138. [7M]
- b) Write down the behavioral VHDL architecture for fixed point to floating point conversion with rounding? [7M]
6. a) Draw the logic diagram of 74x74 IC and explain the operation. Develop the VHDL model for this IC. [7M]
- b) Write down the VHDL code for an n-bit left to right shift register. [7M]

7. a) Explain the state equivalence and machine equivalence with reference to sequential machines. [7M]
- b) Reduce the number of states in the state table, and tabulate the reduced state table [7M] and give proper assignment.

PS	NS,Z	
	X=0	X=1
A	F, 0	B, 0
B	D, 0	C, 0
C	F, 0	E, 0
D	G, 1	A, 0
E	D, 0	C, 0
F	F, 1	B, 1
G	G, 0	H, 0
H	G, 1	A, 0



III B. Tech I Semester Regular/Supplementary Examinations, October/November - 2019
DIGITAL IC APPLICATIONS

(Common to Electronics and Communication Engineering, Electronics and Instrumentation
 Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70


- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**

PART -A**(14 Marks)**

1. a) What is transition time? How it is different from propagation time? [2M]
- b) List out the different data types in VHDL. [3M]
- c) What are the assignment statements in VHDL? [2M]
- d) What do you mean encoder? [2M]
- e) Draw the connection diagram for IC 7490. [3M]
- f) What is state table? [2M]

PART -B**(56 Marks)**

 2. a) Draw the circuit diagram and functional table of ECL 10K 2-input OR/NOR gate and explain its operation. [7M]
- b) Construct a circuit with CMOS as a driver and TTL as a load? Explain the interfacing operation. [7M]
3. a) What are the various types of objects in VHDL and explain? [7M]
- b) What is the use of library clause and use clause? Give examples. [7M]
4. a) Explain the logic synthesis process with suitable block diagram? [7M]
- b) Explain IF statement in VHDL with example. Give the comparisons between CASE and IF statement. [7M]
5. a) What is multiplexer? Draw the logic diagram of 8 to 1 line multiplexer. [7M]
- b) Write a behavioral VHDL program for a dual priority encoder. [7M]
6. a) Explain the operation of a 4-bit synchronous binary counter with the required diagram and waveforms. [7M]
- b) Write VHDL code for 4-bit serial-In Parallel-out register. [7M]
7. a) With suitable example explain the Mealy and Moore models? [7M]
- b) Explain One hot encoding with a suitable example. [7M]



III B. Tech I Semester Regular/Supplementary Examinations, October/November - 2019
DIGITAL IC APPLICATIONS

(Common to Electronics and Communication Engineering, Electronics and Instrumentation
 Engineering, Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **FOUR** Questions from **Part-B**

PART -A**(14 Marks)**

1. a) Explain the difference between static and dynamic power consumption. [2M]
- b) Write the acronym for VHDL. [2M]
- c) What do you mean by sequential statements? [2M]
- d) What is decoder? [3M]
- e) Draw the pin diagram of IC 7495. [3M]
- f) What is state diagram? [2M]

PART -B**(56 Marks)**

2. a) What is steady-state behavior? Explain the different voltage parameters, current parameters and noise margins for CMOS devices. [7M]
- b) Analyze the fall time CMOS inverter output with $R_L = 100\Omega$, $V_L = 2.5V$ and $C_L = 10pF$. Assume V_L as stable state voltage. [7M]
3. a) What is subprogram? Give the syntax of VHDL functions. [7M]
- b) List out the differences between VHDL functions and procedures with example. [7M]
4. a) Explain the following statements with examples: [7M]
 - i) IF statement
 - ii) EXIT statement
 - iii) Assert Statement
 - iv) Report Statement.
- b) Explain the concept of Inertial Delay Model along with one example. [7M]
5. a) Design a barrel shifter for 8-bit using three control inputs. Write a VHDL program for the same in data flow style. [7M]
- b) Using a process statement write a VHDL source code for 4 to 1 multiplexer. [7M]
6. a) List the basic types of shift registers in terms of data movement with diagrams. [7M]
- b) Explain the difference between D-Latch and D-Flip flop using the process block in VHDL. [7M]
7. a) Draw the Mealy and Moore type FSM for serial adder. [7M]
- b) Write down the VHDL code for serial adder. [7M]
